



## How to Build a Simple Electrical Circuit

This quick guide will help you assemble a basic battery-and-bulb circuit using the same components featured in the *Smart Energy Academy* classroom activity,

### Who Turned Out the Lights?

This is a safe, low-voltage activity perfect for primary school students learning about how electricity flows and how energy is transferred.

### What You Will Need

You can use your school's science resources or source inexpensive components from suppliers such as Jaycar, Officeworks, Kmart, or online education suppliers.

#### Basic Circuit Kit:

- **1 × AA battery** (1.5V)
- **1 × battery holder** (optional but recommended)
- **2 × insulated wires** with crocodile clips (red and black ideal)
- **1 × small light bulb** (1.5V–3V recommended)
- **1 × bulb holder**

#### Optional (but helpful):

- Small on/off switch
- Extra wires for longer circuits
- LED (with resistor)

## What Are We Building?

A **simple electrical circuit** that allows electricity to flow from the battery → through the wires → into the bulb → and back to the battery.

When the circuit is complete, the bulb lights up, showing that energy is being transferred and transformed.

## Step-by-step instructions

### 1. Prepare your components

Lay out the battery, bulb holder, bulb, and wires on a desk.

### 2. Insert the bulb

Place the small bulb into the bulb holder. Make sure it is sitting firmly.

### 3. Connect the first wire

Attach one end of a crocodile-clip wire to **one side of the bulb holder**.

Clip the other end to the **positive (+) end of the AA battery** or battery holder.

### 4. Connect the second wire

Attach the second wire to the **other side of the bulb holder**.

Clip the remaining end to the **negative (-) end of the AA battery**.

### 5. Check your circuit

The bulb should now light up.

If not:

- Make sure the wires are clipped to metal parts
- Ensure the bulb is tightly seated
- Check that the battery has charge
- Ensure the clips are not touching each other

## How it works

Electricity flows in a **loop**, called a **circuit**.

For the bulb to light:

- The **circuit must be complete**
- The **battery** supplies electrical energy
- The **wires** carry the electric charge
- The **bulb** transforms the electrical energy into light (and a small amount of heat)

If the loop is broken anywhere, the light goes out.

## Safety tips

Low-voltage circuits like this are very safe, but always follow these guidelines:

- Only use **1.5V–3V bulbs and batteries**
- Do **not** connect batteries directly together to increase voltage
- Ensure wires have **insulated plastic covering**
- Teachers should handle battery changes
- Do not allow students to place wires near mouths or eyes
- Pack away components after use

## Where to Source Components

Affordable kits can be found at:

- **Jaycar**
- **Officeworks**
- **Kmart** (basic science kits)
- **Amazon Australia**
- **School science supply companies** such as Modern Teaching Aids

## Try These Extensions

These optional challenges extend learning for Years 3–6:

### 1. Add a switch

Place a switch between one of the wires and the battery. Students can now *control* the flow of electricity.

### 2. Test different bulbs

Compare brightness between incandescent bulbs and LEDs.

### 3. Build a series circuit

Add a second bulb in line and observe what happens.

### 4. Explore energy transfer

Ask: *Does the bulb get warm? Why?*